

# Circuit with Dependent Sources

Tapas Kumar Bhattacharya

Department of Electrical Engineering  
I.I.T Kharagpur

October 23, 2017

## **Contents**

<b>1</b>	<b>Introduction</b>	<b>3</b>
<b>2</b>	<b>Example</b>	<b>3</b>

TAPAS

# 1 Introduction

We know *Independent* sources ( voltage or current) are those sources whose characteristic remains same no matter in which circuit has it been connected. In a circuit there may exist *dependent* voltage or current sources or both. The magnitude or strength of such sources depends on voltage or current of some other branches. Figure 1 shows the symbol of a dependent voltage source and a dependent current source. For the voltage source shown, magnitude of the voltage across the terminals AB is  $5 \times i_1$  where  $i_1$  is the current in some branch. Similarly for the current source. In a transistor operating in active region, collector current  $I_c$  depends on base current  $I_b$  and in the collector circuit we can think a current source is present of value  $\beta I_b$ . In mutually coupled coils, current  $i_1$  of coil-1 causes a voltage source to be present in coil-2 and magnitude of the voltage is  $M \frac{di_1}{dt}$ .

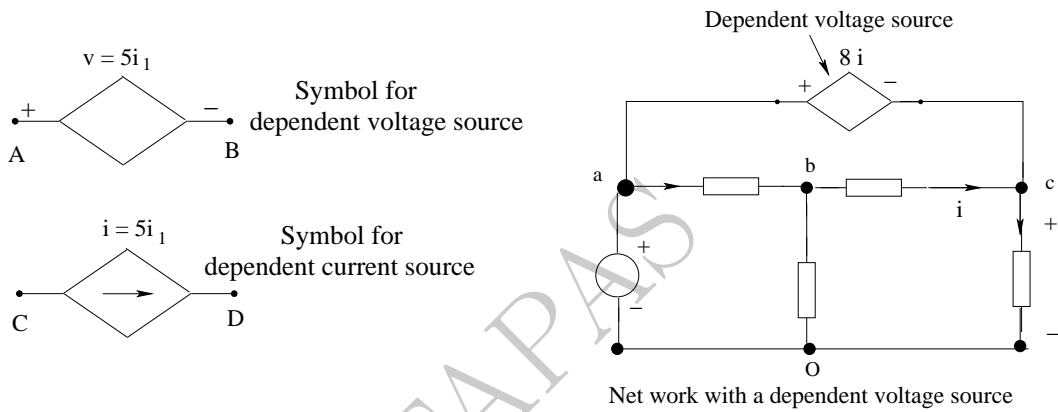


Figure 1: Symbols for dependent source

In this note, we shall analyze circuit having both independent and dependent sources. Since KVL and KCL must be satisfied, so any known method can be used to analyze such circuits. You should however be careful to calculate  $V_{th}$  and  $R_{th}$  of such circuit. Go through the following solved example to understand how to handle such circuit.

## 2 Example

Consider the network shown in figure 2. We have to calculate the current  $i_2$  flowing through the  $2\Omega$  resistance.

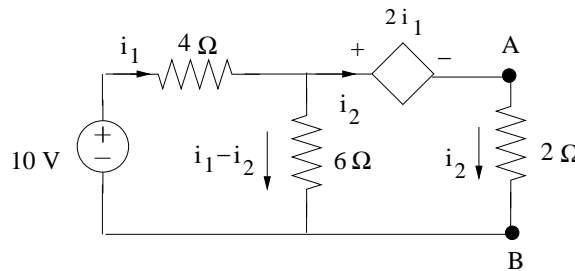


Figure 2:

$$\begin{aligned} \text{KVL in left hand mesh: } 4i_1 + 6(i_1 - i_2) &= 10 \\ \text{or, } 10i_1 - 6i_2 &= 10 \end{aligned}$$

$$\begin{aligned}
 \text{KVL in the over all outer loop: } 4i_1 + 2i_1 + 2i_2 &= 10 \\
 \text{or, } 6i_1 + 2i_2 &= 10 \\
 \text{solving we get, } i_2 &= \frac{5}{7} \text{ A}
 \end{aligned}$$

Suppose we want to get  $i_2$  by applying Thevenin theorem. To calculate Thevenin voltage we have to remove  $2\Omega$  and calculate open circuit voltage across A and B i.e.,  $V_{th} = V_{AB}|_{O.C}$ . Refer to figure 3(a) to calculate  $V_{th}$ . As can be seen  $V_{th} = 6 \times 1 - 2 = 4 \text{ V}$ .

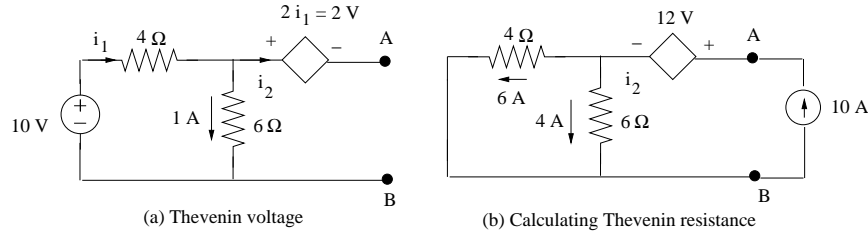


Figure 3:

To calculate the Thevenin resistance across A & B one has to follow the following steps.

1. Deactivate the independent sources as usual i.e, short circuit the independent voltage sources and open circuit the independent current sources.
2. Keep all the dependent sources in the circuit.
3. Excite the circuit from terminals A & B with a known external voltage source  $V$  and solve the circuit to calculate the current drawn  $I$  from from  $V$ . Ratio of  $V$  and  $I$  gives  $R_{th}$ .
4. Alternatively you can excite the circuit by a known current source  $I$  from A & B and solve the circuit to calculate  $V_{AB}$ . The ratio of  $V_{AB}$  and  $I$  will also give  $R_{th}$ .

For the present problem we excited the circuit with a 10 A current source from terminals AB and replaced the independent source 10 V by short circuit without disturbing the dependent voltage source  $2i_1$  as shown in figure 3(b). Current in the  $6\Omega$  resistor is  $10 \times \frac{6}{(4+6)} = 6 \text{ A}$ . So  $V_{AB} = 4 \times 6 + 12 = 36 \text{ V}$ . Therefore,  $R_{th} = 36/10 = 3.6\Omega$ . We already know  $V_{th} = 4V$ . Current through the  $2\Omega$  resistance in the original circuit is  $i_2 = 4/(3.6 + 2) = 5/7 \text{ A}$ . The result obtained is same as obtained earlier by KVL method.