

Tutorial 8 Solution

① Branches → ① ② ③ ④ ⑤ ⑥ ⑦ ⑧


$$A = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \end{bmatrix}$$

Observe that the sum of all the rows is not zero.
(In other words some columns do not have both +1 and -1.) Therefore, the given matrix must be the reduced incidence matrix. We can therefore write the complete incidence matrix as


$$A = \begin{array}{ccccccccc} & \text{①} & \text{②} & \text{③} & \text{④} & \text{⑤} & \text{⑥} & \text{⑦} & \text{⑧} & \text{Branches} \\ \begin{matrix} \text{①} \\ \text{②} \\ \text{③} \\ \text{④} \\ \text{⑤} \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \\ -1 & -1 & -1 & -1 & 0 & 0 & 0 & 0 \end{bmatrix} & \begin{matrix} -1 \\ -2 \\ -3 \\ -4 \\ -5 \end{matrix} \end{array}$$

↑
Nodes

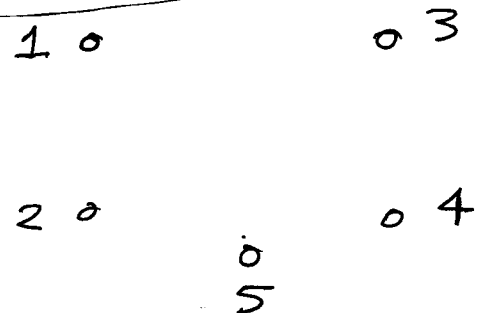
There are 5 nodes
and 8 edges
We first draw the
5 nodes arbitrarily



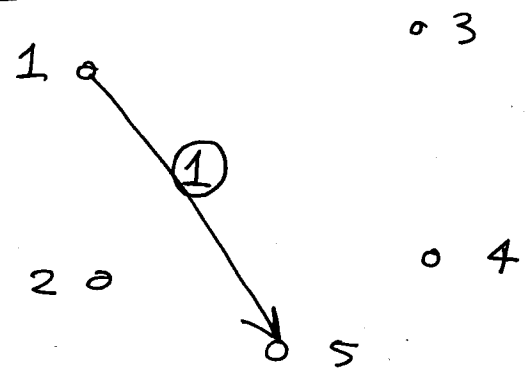
Then observe that branch
① starts at node 1
and stops at node 5
(observe the first column)
So we can draw branch ①



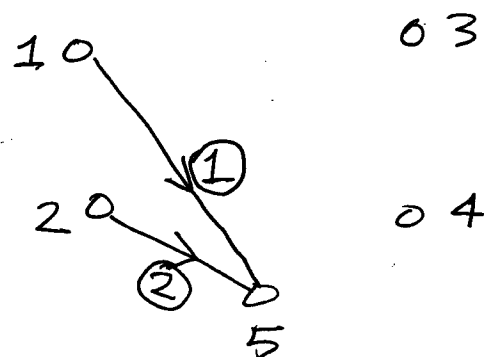Similarly branch ② starts
at node 2 and stops
at node 5



In this way we can draw all the branches

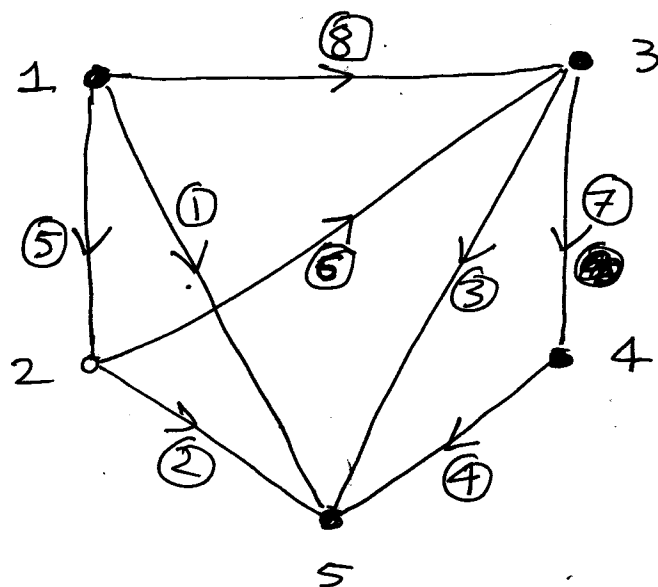

To distinguish node numbers from edge numbers, edge numbers are circled.

②



$$Q = \begin{bmatrix} 1 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 & 0 & 1 & 0 \end{bmatrix} \begin{matrix} -1 \\ -2 \\ -3 \\ -4 \end{matrix}$$

cut sets


Branches → ① ② ③ ④ ⑤ ⑥ ⑦

Note that branch ①, ②, ③, ④ are present in only cutsets 1, 2, 3, 4 respectively. Therefore ①, ②, ③, ④ are the twigs of the underlying tree. So ⑤, ⑥ & ⑦ are the links.

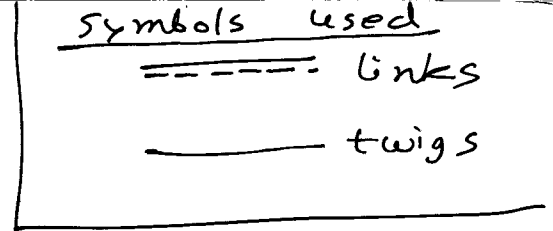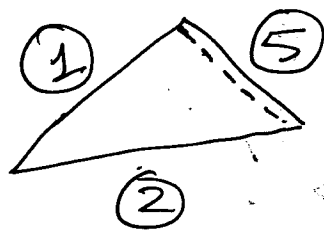
Now branch ⑤ is present in ~~two~~ cutsets 1 & 2. Therefore branches ⑤, ① & ② should form a loop.



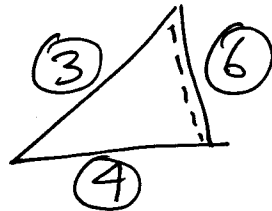
Similarly, branch ⑥ is present in cutsets 3 and 4. Therefore branches ⑥, ③ & ④ should form a loop



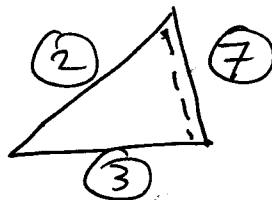Similarly branches ⑦, ② and ③ will form a loop.




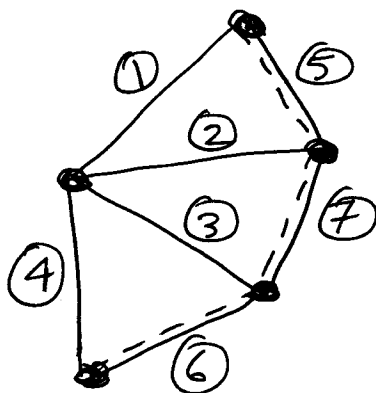Now if we cleverly combine the above three figures we will get




Now we have to put the arrows consistently with the \mathcal{Q} matrix


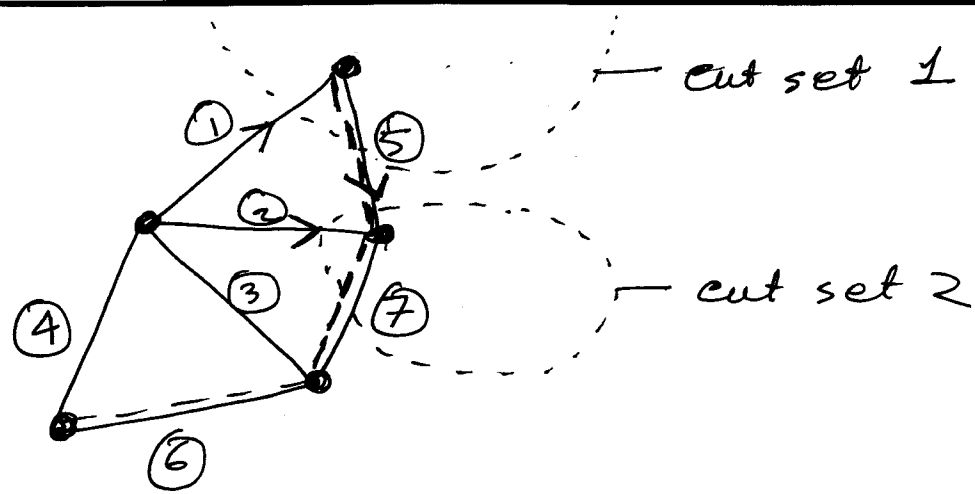
From column ⑤ of \mathcal{Q} , we can say ^{with respect to cutset 1} ⑤ and ① are in opposite direction, but ⑤ and ② are in same direction ^{with respect to cutset 2}



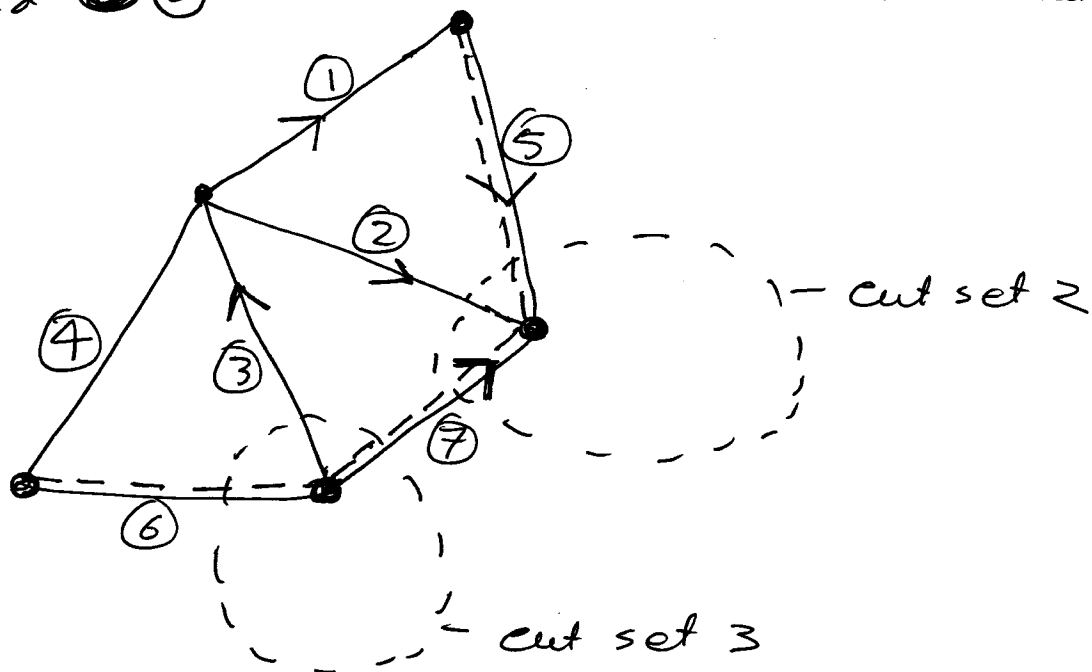
From column ~~7~~ of \mathcal{A} we can say
~~7~~ and ~~2~~ are in same direction with respect to cutset 2
~~7~~ and ~~3~~ are in same direction with respect to cutset 3



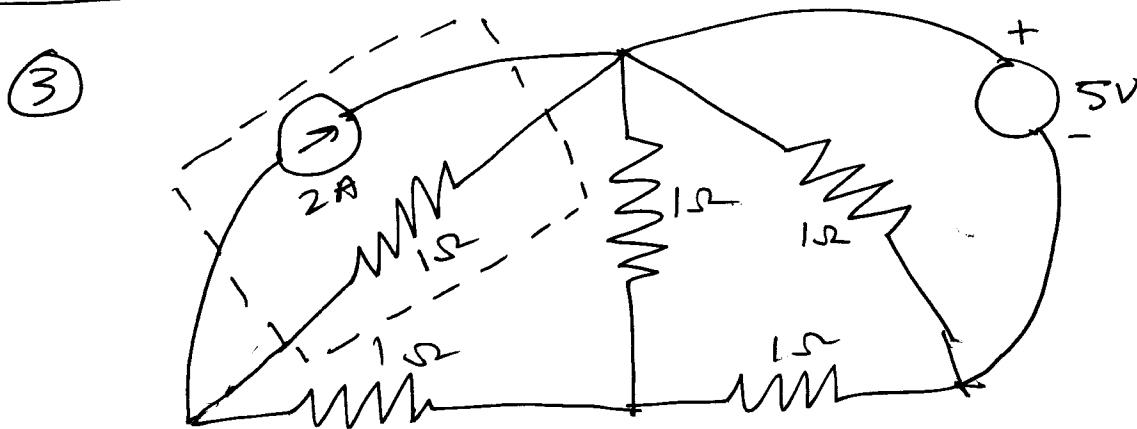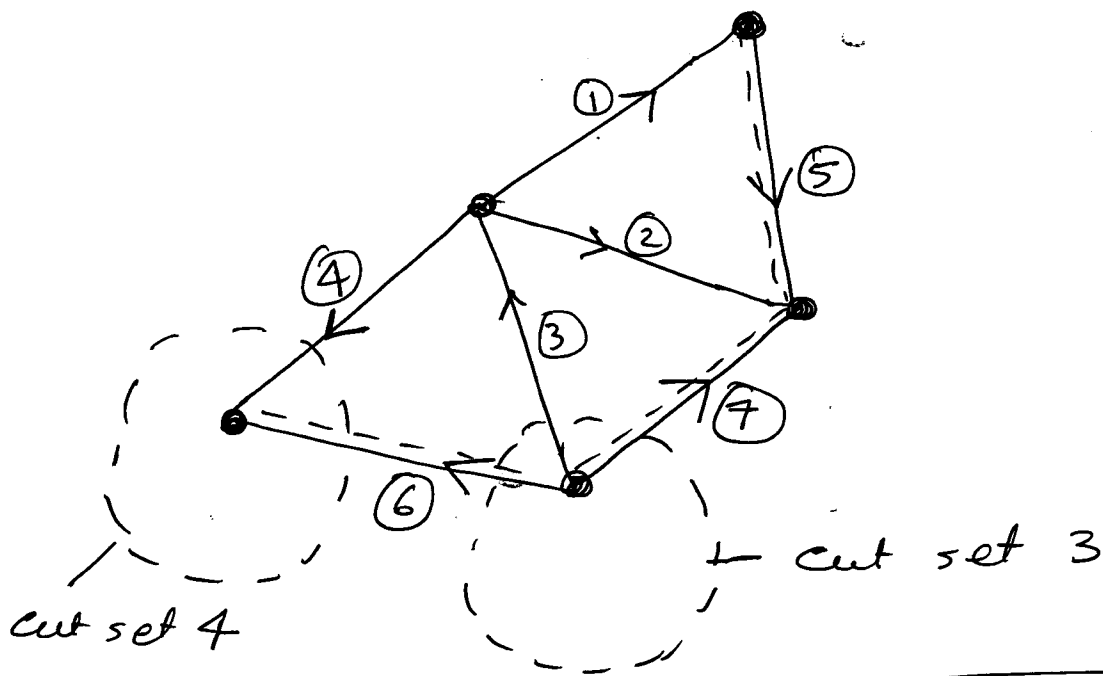
Finally from column ~~6~~ of \mathcal{A} we see that
~~6~~ & ~~3~~ are in same direction with respect to cutset 3
~~6~~ & ~~4~~ are in same direction with respect to cutset 4



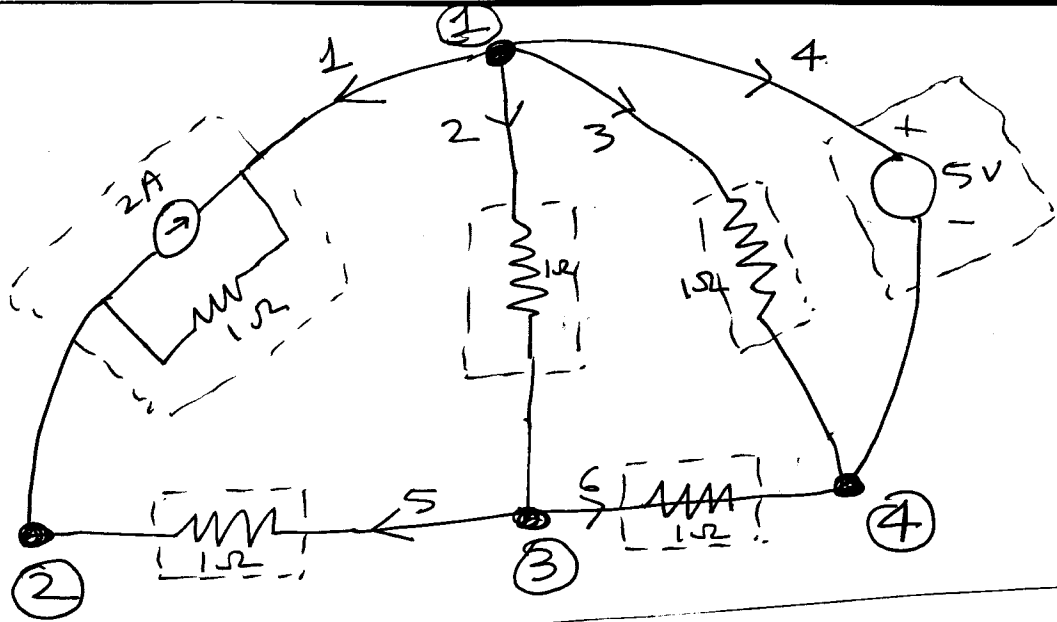
Since we have to use mesh analysis if we treat the current source alone as an independent branch then the ~~total~~ ~~admi~~ impedance of that branch will be infinite (∞). We will not be able to solve the problem. So we will treat the current source together with its adjacent ^(parallel) ~~branch~~ 1Ω resistance as a single branch.



Node numbers are in circle

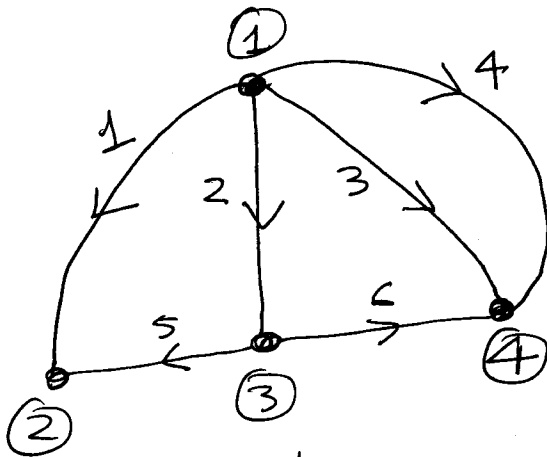

graph.

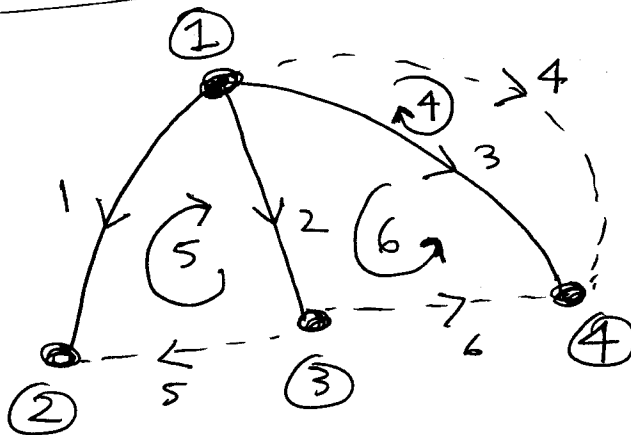

Tree and loops

Symbols

— twigs

--- links


G loops

Note that twigs are numbered first & then the links

B =

Edges →	1	2	3	4	5	6
4	0	0	-1	+1	0	0
5	-1	+1	0	0	+1	0
6	0	+1	-1	0	0	+1

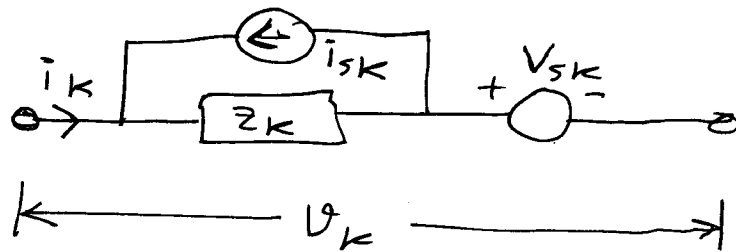Now the general structure of a branch can be chosen as



Therefore, $V_k = (i_k + i_{sk})Z_k + V_{sk}$

considering all edges we can write

$$\begin{bmatrix} V_k \\ | \\ | \end{bmatrix} = \begin{bmatrix} Z_k \\ | \\ | \end{bmatrix} \left(\begin{bmatrix} i_k \\ | \\ | \end{bmatrix} + \begin{bmatrix} i_{sk} \\ | \\ | \end{bmatrix} \right) + \begin{bmatrix} V_{sk} \\ | \\ | \end{bmatrix}$$

For the given graph

$$Z_k = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} i_{sk} \\ | \\ | \end{bmatrix} = \begin{bmatrix} +2 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \text{and} \quad \begin{bmatrix} V_{sk} \\ | \\ | \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ +5 \\ 0 \\ 0 \end{bmatrix}$$

[carefully consider the polarities of sources & corresponding \pm sign]

$$\text{Now } [V_k] = [Z_k] \left([i_k] + [i_{sk}] \right) + [V_{sk}]$$

Multiplying both side with B

$$\Rightarrow B[V_k] = B[Z_k] \left([i_k] + [i_{sk}] \right) + B[V_{sk}]$$

$= 0$

$$[\because B[V_k] = 0 \text{ (KVL)}]$$

$$\therefore B[Z_k][i_k] = -B[V_{sk}] - B[Z_k][i_{sk}]$$

$$\Rightarrow B[Z_k]B^T[i_L] = -B[V_{sk}] - B[Z_k][i_{sk}]$$

$$\text{Where } [i_L] = \begin{bmatrix} i_{L4} \\ i_{L5} \\ i_{L6} \end{bmatrix} = \text{loop currents}$$

Now let us put the values of B, $[Z_k]$, $[V_{sk}]$, $[i_{sk}]$ etc.

$$\text{RHS} = -B[V_{sk}] - B[Z_k][i_{sk}]$$

$$= -B \left(\begin{bmatrix} 0 \\ 0 \\ 0 \\ 5 \\ 2 \end{bmatrix} - \begin{bmatrix} 1 & & & & \\ & 1 & & & \\ & & 1 & & \\ & & & 0 & \\ & & & & 1 \end{bmatrix} \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \right)$$

$$= -B \left(\begin{bmatrix} 0 \\ 0 \\ 0 \\ 5 \\ 0 \\ 0 \end{bmatrix} - \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \right) = -B \begin{bmatrix} -2 \\ 0 \\ 0 \\ 5 \\ 0 \\ 0 \end{bmatrix}$$

$$= \begin{bmatrix} -5 \\ +2 \\ 0 \end{bmatrix} \quad (\text{putting the value of } B)$$

$$\text{Now } B [Z_K] B^T = B \begin{bmatrix} 1 & & & & & \\ & 1 & & & & \\ & & 1 & & & \\ & & & 0 & & \\ & & & & 1 & \\ & & & & & 1 \end{bmatrix} \begin{bmatrix} 0 & -1 & 0 \\ 0 & 1 & 1 \\ -1 & 0 & -1 \\ 1 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 0 & 0 & -1 & 1 & 0 & 0 \\ -1 & 1 & 0 & 0 & 1 & 0 \\ 0 & 1 & -1 & 0 & 0 & 1 \end{bmatrix} \times \begin{bmatrix} 0 & -1 & 0 \\ 0 & 1 & 1 \\ -1 & 0 & -1 \\ 0 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} +1 & 0 & 1 \\ 0 & 3 & 1 \\ +1 & 1 & 3 \end{bmatrix}$$

$$\therefore \begin{bmatrix} +1 & 0 & 1 \\ 0 & 3 & 1 \\ +1 & 1 & 3 \end{bmatrix} [i_L] = \begin{bmatrix} -5 \\ +2 \\ 0 \end{bmatrix}$$

You may now use a matrix inversion or solve the equations in any other manner

$$\begin{aligned} +i_{L1} + i_{L3} &= -5 \\ 3i_{L5} + i_{L3} &= 2 \\ -i_{L1} + i_{L2} &= 0 \Rightarrow i_{L1} = i_{L2} \end{aligned}$$

$$\Rightarrow i_{L4} + i_{L6} = -5 \quad \text{--- (i)}$$

$$3i_{L5} + i_{L6} = 2 \quad \text{--- (ii)}$$

$$i_{L4} + i_{L5} + 3i_{L6} = 0 \quad \text{--- (iii)}$$

$$\textcircled{iii} - \textcircled{i} - 2\textcircled{ii} \Rightarrow -5i_{L5} = 1 \Rightarrow i_{L5} = -\frac{1}{5}$$

$$\therefore i_{L6} = 2 + \frac{3}{5} = \frac{13}{5}$$

$$\text{and } i_{L4} = \frac{1}{5} - \frac{39}{5} = -\frac{38}{5}$$

Now the branch voltages and currents can be found easily


⑥

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} \textcircled{1} \\ \textcircled{2} \\ \textcircled{3} \\ \textcircled{4} \\ \textcircled{5} \end{matrix} & \begin{bmatrix} 1 & & & & 1 & & & 1 \\ & 1 & & & -1 & 1 & & \\ & & 1 & & & -1 & 1 & -1 \\ & & & 1 & & & -1 & \\ -1 & -1 & -1 & -1 & & & & \end{bmatrix} \end{matrix}$$

Branch voltages in terms of node voltages

$$\begin{bmatrix} V_{e1} \\ V_{e2} \\ V_{e3} \\ V_{e4} \\ V_{e5} \\ V_{e6} \\ V_{e7} \\ V_{e8} \end{bmatrix} = A^T \begin{bmatrix} V_{n1} \\ V_{n2} \\ V_{n3} \\ V_{n4} \\ V_{n5} \end{bmatrix}$$

Chosen tree and loops

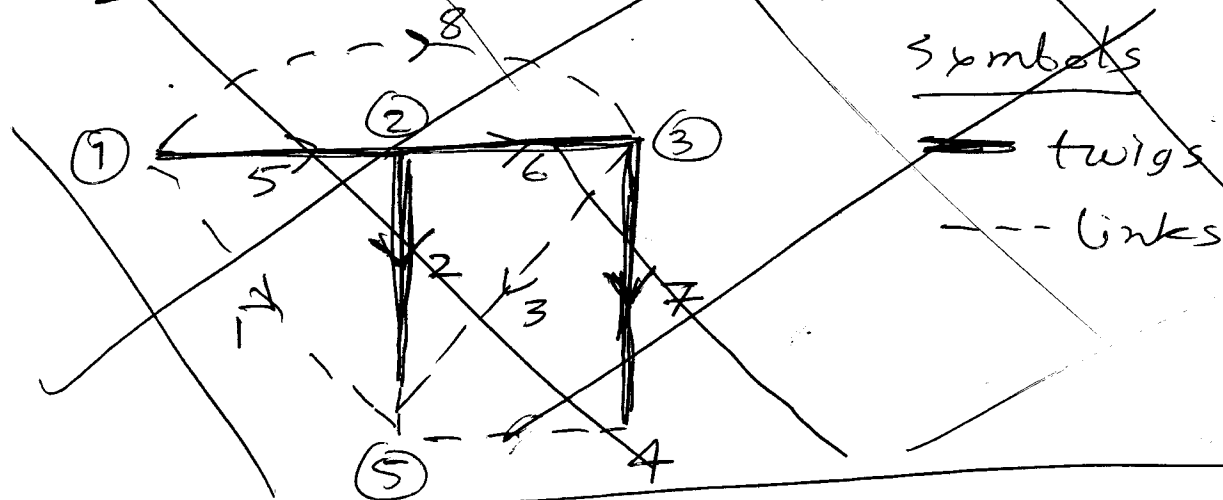


Symbols

— twigs

--- links

Tree and loops

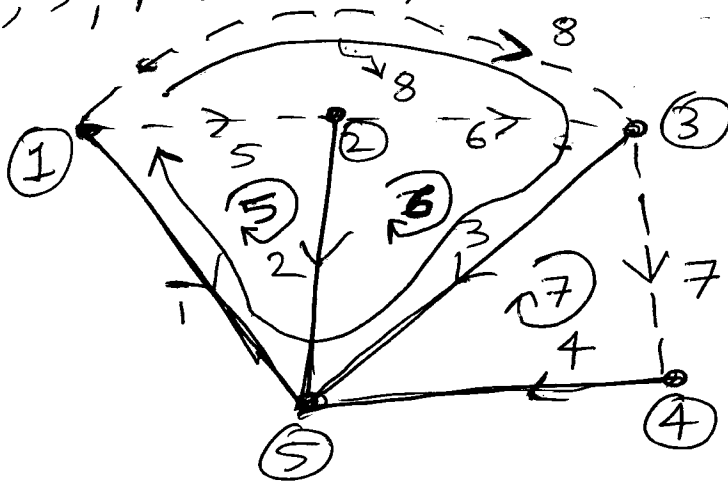You may choose any tree of your choice for this problem. But note that edges 1, 2, 3, 4 (i.e. the first 4 edges form a tree). So I am choosing 1, 2, 3, 4 as my tree.




$\therefore B =$


	1	2	3	4	5	6	7	8
5	-1	+1			+1			
6		-1	+1			+1		
7			-1	+1			+1	
8	-1		+1					+1

Branch currents in terms of loop currents
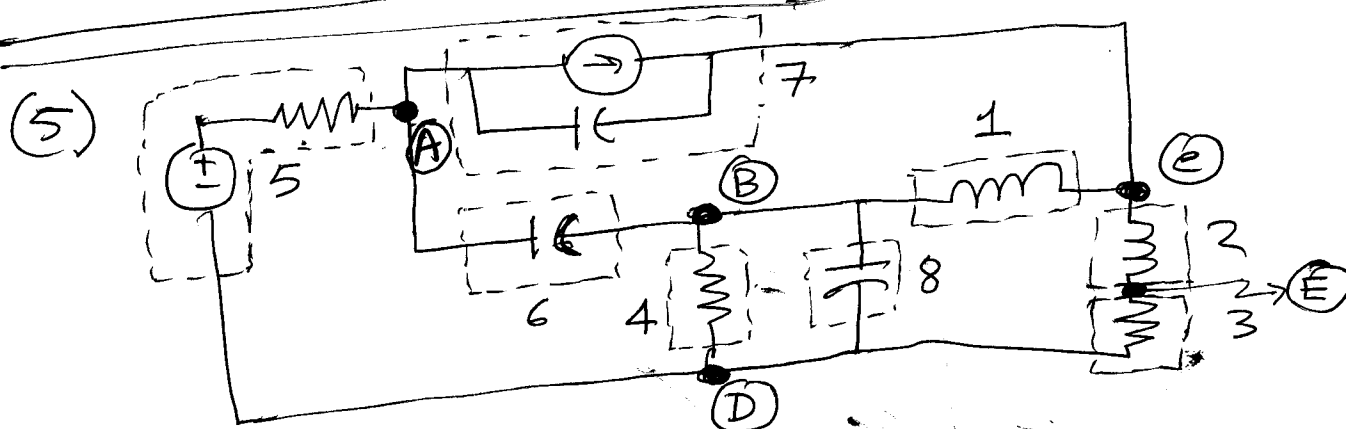
$$\begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \\ i_{e7} \\ i_{e8} \end{bmatrix} = B^T \begin{bmatrix} i_{L5} \\ i_{L6} \\ i_{L7} \\ i_{L8} \end{bmatrix}$$




Graph

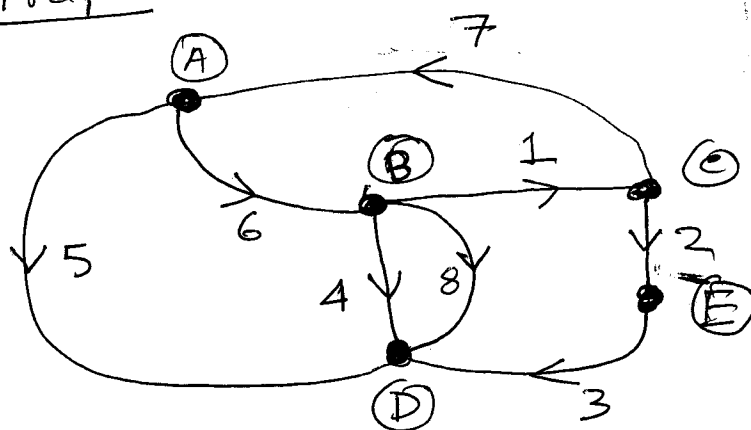

Note that Node E is unnecessary, but since edge 2 and 3 are given as 2 different edges in the question, we are following it.

Tree

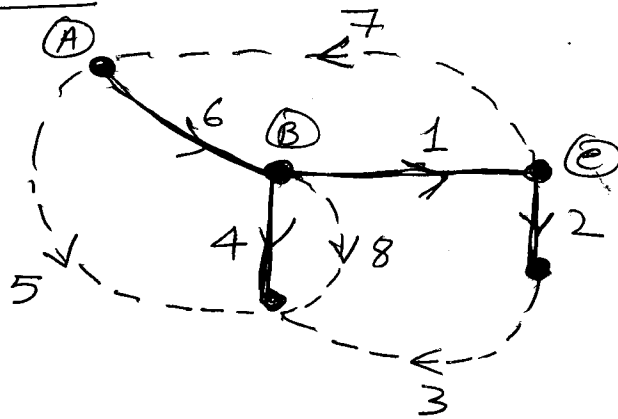

Since the edge numbers are already given in the question we are not able to name the twigs first and the the links.

Cutset matrix

$$Q = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 4 \\ 6 \end{matrix} & \begin{bmatrix} +1 & 0 & -1 & 0 & 0 & 0 & -1 & 0 \\ 0 & +1 & -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & +1 & +1 & +1 & 0 & 0 & +1 \\ 0 & 0 & 0 & 0 & +1 & +1 & -1 & 0 \end{bmatrix} \end{matrix}$$

Relation between twig and branch voltages


$$\begin{bmatrix} V_{e1} \\ V_{e2} \\ V_{e3} \\ V_{e4} \\ V_{e5} \\ V_{e6} \\ V_{e7} \\ V_{e8} \end{bmatrix} = Q^T \begin{bmatrix} V_{e1} \\ V_{e2} \\ V_{e4} \\ V_{e6} \end{bmatrix}$$

KCL

$$Q \begin{bmatrix} V_{e1} \\ V_{e2} \\ V_{e3} \\ \vdots \\ V_{e8} \end{bmatrix} = 0$$

Circuit equations

Chosen general structure of any branch

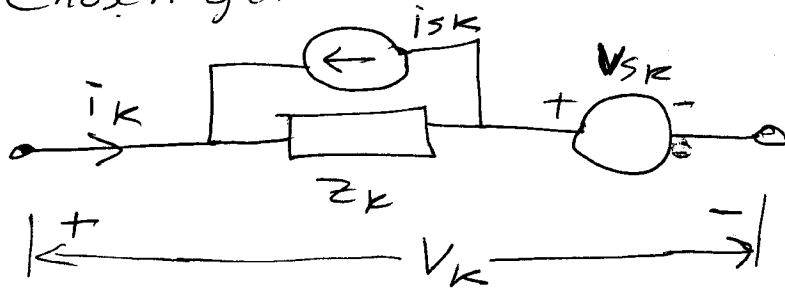

$$\therefore i_k = (V_k - V_{sk}) / Z_k - i_{sk}$$

$$= Y_k (V_k - V_{sk}) - i_{sk}$$

$$[\text{where } Y_k = \frac{1}{Z_k}]$$

For all branches

$$[i_k] = [Y_k] ([V_k] - [V_{sk}]) - [i_{sk}]$$

$$\Rightarrow Q[i_k] = 0 = Q[Y_k] ([V_k] - [V_{sk}]) - Q[i_{sk}]$$

$$\Rightarrow Q[Y_k][V_k] = Q[Y_k][V_{sk}] + Q[i_{sk}]$$

$$\begin{aligned} \Rightarrow Q[Y_k] Q^T [\text{twig voltages}] &= Q[Y_k][V_{sk}] + Q[i_{sk}] \\ &= Q([Y_k][V_{sk}] + [i_{sk}]) \end{aligned}$$

For the given graph

$$[V_{sk}] = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\text{and } [i_{sk}] = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

[be careful about the \pm sign]

Θ is derived before

and $[Y_k] =$

$1/L_1 S$	0	0	0	0	0	0	0
0	$1/L_2 S$	0	0	0	0	0	0
0	0	$1/R_3$	0	0	0	0	0
0	0	0	$1/R_4$	0	0	0	0
0	0	0	0	$1/R_5$	0	0	0
0	0	0	0	0	$C_6 S$	0	0
0	0	0	0	0	0	$C_7 S$	0
0	0	0	0	0	0	0	$C_8 S$


and $[\text{twig voltages}] =$

V_{e1}
V_{e2}
V_{e4}
V_{e6}


And the nodal equation is

$$\Theta [Y_k] \Theta^T [\text{twig voltages}] = \Theta ([Y_k] [V_{sk}] + [i_{sk}])$$

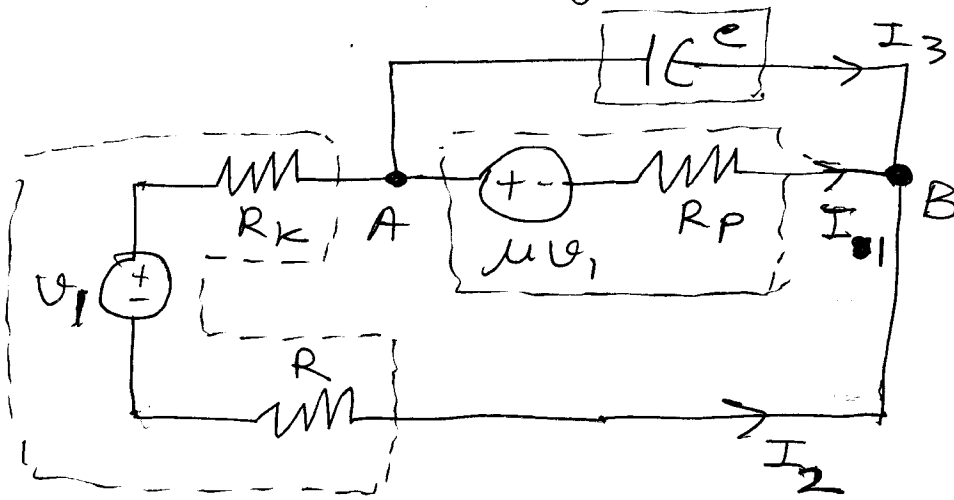
④ To make the solution simpler let us change the branch and node numberings from what is given in the question.



Graph

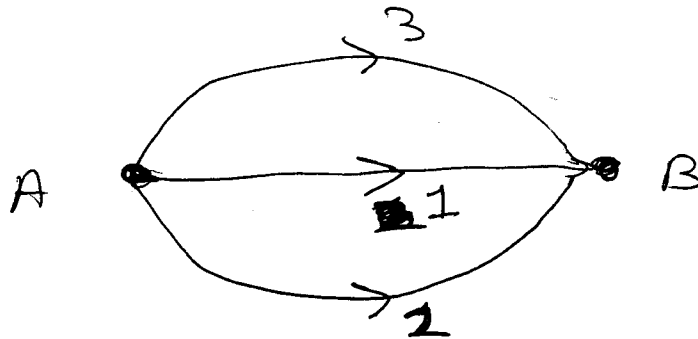

Tree and loops

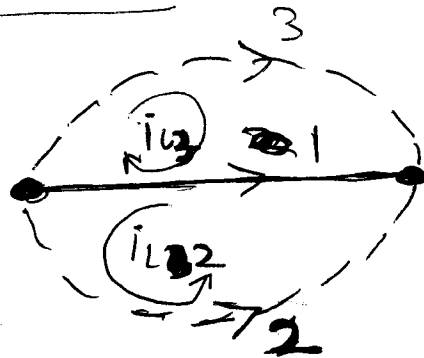

Loop matrix

$$B = \begin{matrix} & \begin{matrix} 1 & 2 & 3 \end{matrix} \\ \begin{matrix} 1 \\ 2 \end{matrix} & \left[\begin{array}{c|c|c} -1 & +1 & 0 \\ -1 & 0 & +1 \end{array} \right] \end{matrix}$$

Branch impedance matrix


$$[Z_k] = \begin{bmatrix} R_p & 0 & 0 \\ 0 & R+R_k & 0 \\ 0 & 0 & \frac{1}{Cs} \end{bmatrix}$$

Source voltage matrix

$$[V_{sk}] = \begin{bmatrix} \mu V_1 \\ V_1 \\ 0 \end{bmatrix}$$

Loop equation

Chosen general structure of branches

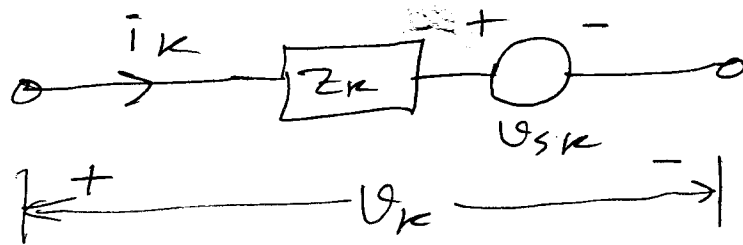

[We need not use a current source, since there is no current source in this problem]

$$V_k = Z_k i_k + V_{sk}$$

$$\Rightarrow [V_k] = [Z_k][i_k] + [V_{sk}]$$

$$\Rightarrow Q[V_k] = 0 = Q[Z_k][i_k] + Q[V_{sk}]$$

$$\Rightarrow Q[Z_k][i_k] = -Q[V_{sk}]$$

$$\Rightarrow Q[Z_k]Q^T [\text{loop currents}] = -Q[V_{sk}]$$

$$\Rightarrow \begin{bmatrix} -1 & 1 & 0 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} R_p & & \\ & R+R_k & \\ & & \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} -1 & -1 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} i_{L_2} \\ i_{L_3} \end{bmatrix}$$

$$= - \begin{bmatrix} -1 & 1 & 0 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} \mu V_1 \\ V_1 \\ 0 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} -1 & 1 & 0 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} -R_p & -R_p \\ R+R_k & 0 \\ 0 & 1/Cs \end{bmatrix} \begin{bmatrix} i_{L_2} \\ i_{L_3} \end{bmatrix} = - \begin{bmatrix} 1-\mu \\ -\mu \end{bmatrix} V_1$$

$$\Rightarrow \begin{bmatrix} R_p+R+R_k & R_p \\ R_p & R_p+\frac{1}{Cs} \end{bmatrix} \begin{bmatrix} i_{L_2} \\ i_{L_3} \end{bmatrix} = - \begin{bmatrix} 1-\mu \\ -\mu \end{bmatrix} V_1 \quad \text{--- (i)}$$

Solution of equation

Matrix inversion may now be difficult so we may do other manipulations. The goal is to find source current only, that means we need only $(-i_{L_2})$

From equation (i) we have

$$\begin{aligned} (R_p+R+R_k)i_{L_2} + R_p i_{L_3} &= -(1-\mu)V_1 \quad \text{--- (ii)} \\ R_p i_{L_2} + (R_p+\frac{1}{Cs})i_{L_3} &= +\mu V_1 \quad \text{--- (iii)} \end{aligned}$$

~~$$\begin{aligned} \text{(ii)} \times R_p / - \text{(iii)} \times (R+R_p+R_k) &\Rightarrow \\ \left(R_p^2 - (R+R_p+R_k)(R_p+\frac{1}{Cs}) \right) i_{L_2} &= (-R_p(1-\mu) + (R+R_p+R_k)\mu) V_1 \end{aligned}$$~~

$$\text{from } \textcircled{ii} \times \left(R_p + \frac{1}{cs}\right) - \textcircled{iii} \times R_p \Rightarrow$$

$$\left((R + R_p + R_k) \left(R_p + \frac{1}{cs}\right) - R_p^2\right) \dot{i}_{L2} = \left((\mu - 1) \left(R_p + \frac{1}{cs}\right) - \mu R_p\right) \dot{v}_1$$

$$\therefore \dot{i}_{L2} = \frac{(\mu - 1) \left(R_p + \frac{1}{cs}\right) - \mu R_p}{(R + R_p + R_k) \left(R_p + \frac{1}{cs}\right) - R_p^2} \dot{v}_1$$

$$\therefore \text{Source current} = -\dot{i}_{L2} = \frac{R_p + \frac{1}{cs} - \mu \left(\frac{1}{cs}\right)}{\left(R_p + \frac{1}{cs}\right)(R + R_p + R_k) - R_p^2}$$

[KINDLY CHECK MY CALCULATION, I AM NOT VERY SURE]

$$\therefore \text{Driving point admittance} = \frac{R_p + \frac{1}{cs} - \mu \left(\frac{1}{cs}\right)}{\left(R_p + \frac{1}{cs}\right)(R + R_p + R_k) - R_p^2}$$
