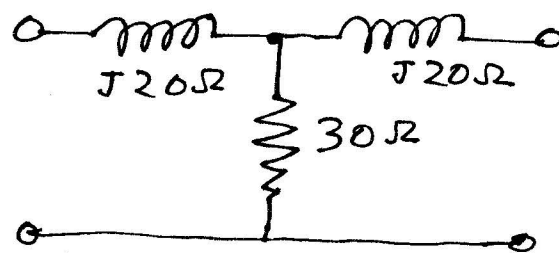



TWO PORT NETWORKS

- 1) Determine the Z and Y parameters of the network below



Is this network reciprocal? Is this network symmetric?

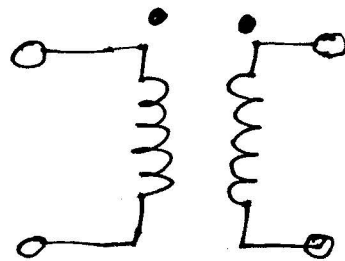- 2) Determine the Z and Y parameters of the following network



$$L_1 = L_2 = 2H$$

$$M = 1H$$


Is the network reciprocal, symmetric?


- 3) Determine the h -parameters with the following data

(i) with output shorted: $V_1 = 25V$, $I_1 = 1A$, $I_2 = 2A$

(ii) with input terminals open-circuited:

$$V_1 = 10V, V_2 = 50V, I_2 = 2A$$

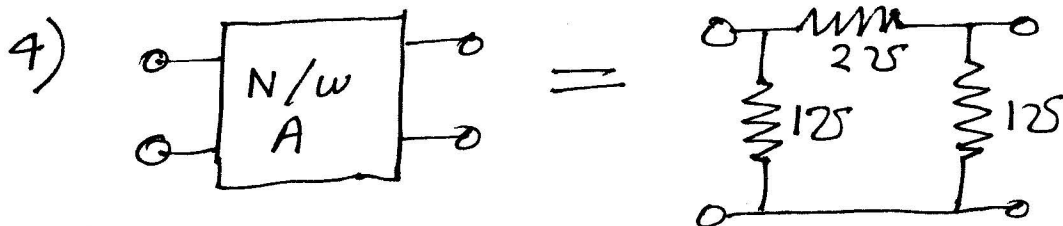

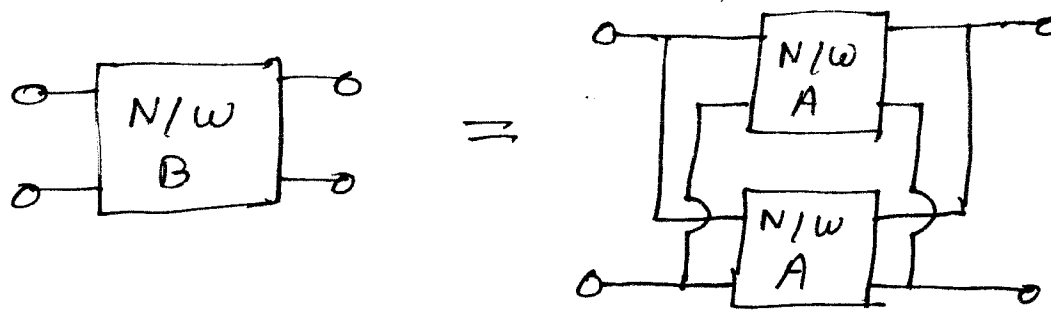

- (a) Find the Y -parameters of N/w A
 (b) Find the Y -parameters of N/w B


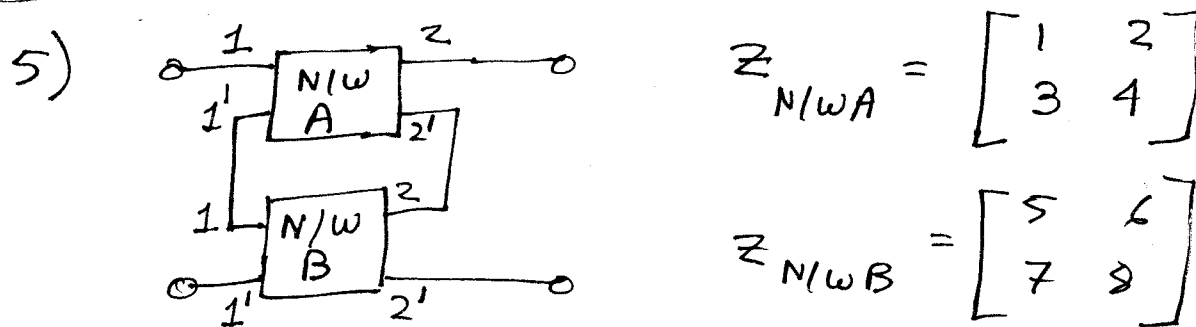


Fig A

Find the Z -parameters of the combined network in Fig A.

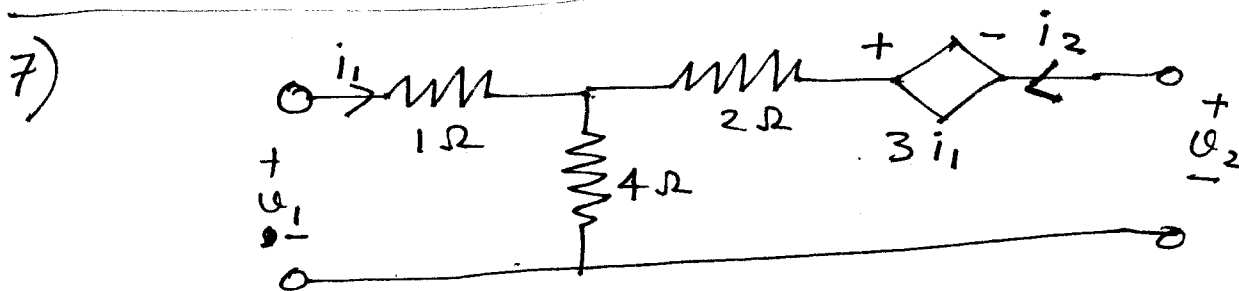6) If $Z = \begin{bmatrix} 2 & 1 \\ 3 & 0 \end{bmatrix}$, $h = ?$




If
$$\begin{bmatrix} V_2 \\ i_2 \end{bmatrix} = \begin{bmatrix} E & F \\ G & H \end{bmatrix} \begin{bmatrix} V_1 \\ -i_1 \end{bmatrix}$$


then $E, F, G, H = ?$

9) Determine Z, h, Y, t parameters of the following network


a)

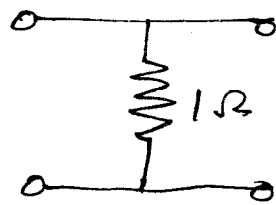


b)

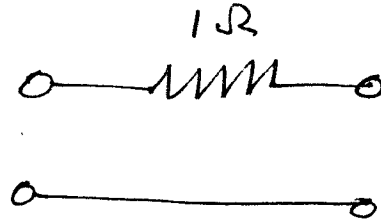

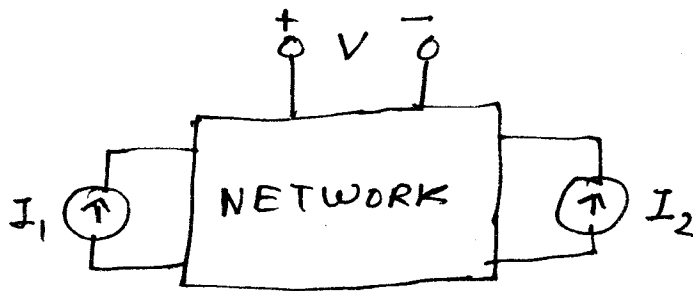10) The linear network shown in Fig below contains only resistors. If $I_1 = 8A$ and $I_2 = 12A$, V is found to be $80V$. However, if $I_1 = -8A$ and $I_2 = 4A$ then $V = 0V$. Find V when $I_1 = I_2 = 20A$




11)

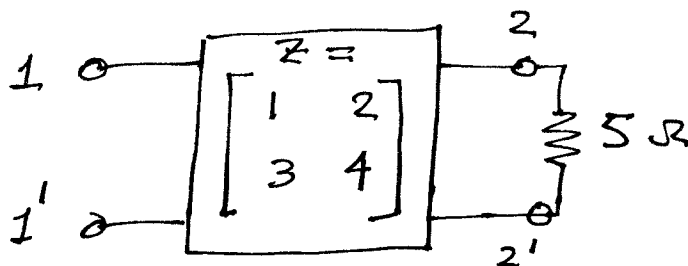

What is the value of driving point impedance of port 1

12)

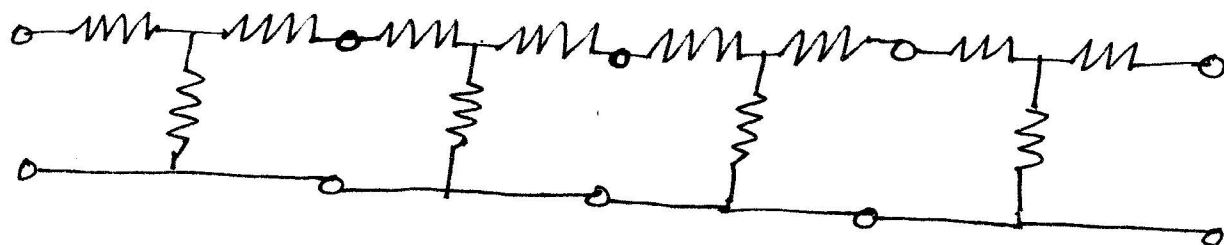


All resistances are 1Ω

Find the ABCD parameters of the above network.

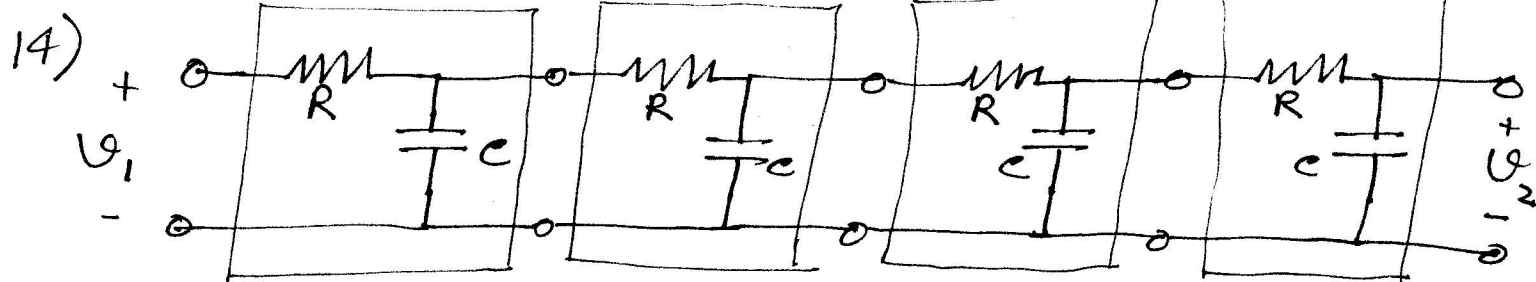13) Construct a two port network (which can contain dependent sources, but no independent source) such that the h -parameters of the network is given by

$$h = \begin{bmatrix} 1\Omega & 1 \\ 100 & .5V \end{bmatrix}$$



If $V_1 = \cos(\omega t)$

Find $|V_2|$ as a function of ω .